Student's Name:

Introduction to circuit analysis


Homework 5 – Series-Parallel Circuit


Instructions:

- YOU HAVE TO SHOW ALL WORK IN ORDER TO RECEIVE FULL CREDIT
- All answer must be in engineering notation rounded off to the hundredth

------ Homework Starts Here ------


1) Determine the total resistance, R_T

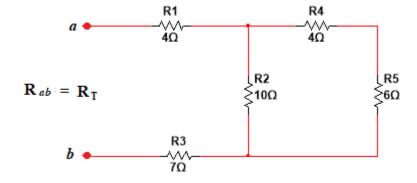

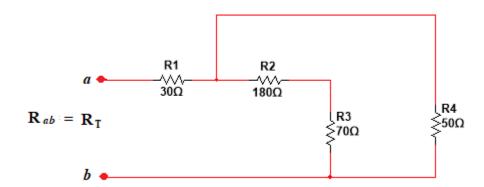


2) For the network

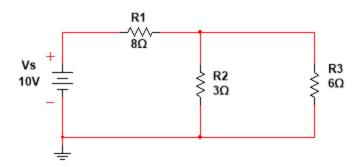- a. Sketch two equivalent circuit
- b. Determine R_T
- c. Find I_{R1}, I_{R2}, and I_{R3}
- d. Find voltage $V_{R1},\,V_{R2},$ and V_{R3}



3) For the following circuit:

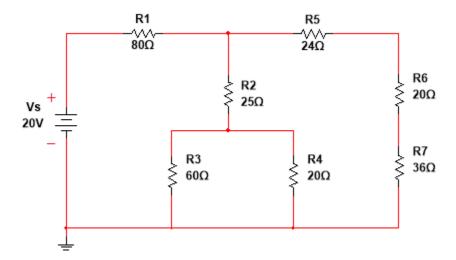

- a. Sketch 3 equivalent circuit
- b. Find the total resistance, R_T
- c. Calculate I_T or I_S
- d. Find the voltage across each resistor

 V_{R6} V_{R7}

e. Find the current through each resistor

 I_{R1}

I_{R2}_____

 I_{R3}


 I_{R4}

 I_{R5}

 I_{R6}

 I_{R7}

4) For the ladder network

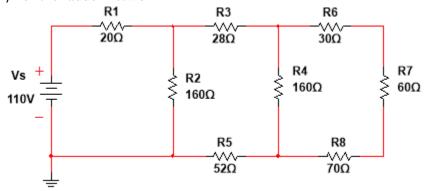

- a. Sketch three equivalent circuit
- b. Determine R_T
- c. Calculate Is
- d. Find the voltage across each resistor

 V_{R1}

 V_{R2}

 V_{R3}

 $V_{R4}\underline{\hspace{1cm}}$

 $V_{R5}____$

 $V_{R6}\underline{\hspace{1cm}}$

 V_{R7}

 V_{R8}

e. Find the current through each resistor

 I_{R1}

 I_{R2}

 I_{R3}

 $I_{R4}\underline{\hspace{1cm}}$

 I_{R5}

 I_{R6}

 I_{R7}

 I_{R8}